

---

## Controlling RGB LED with PWM and Arduino Uno

### Objective:

Mix red, green, and blue light to create different colors by adjusting the brightness of each LED using PWM (Pulse Width Modulation).

### Components Required:

- Arduino Uno
- 1 Common Cathode RGB LED
- 3 Resistors (220Ω–330Ω, one for each color pin)
- Jumper wires & breadboard

### Circuit Overview:

- An RGB LED has **4 pins**:
  - **Common Cathode (GND)**
  - **Red Anode** → PWM pin (e.g., D9) through resistor
  - **Green Anode** → PWM pin (e.g., D10) through resistor
  - **Blue Anode** → PWM pin (e.g., D11) through resistor

### Working Principle:

- **PWM (Pulse Width Modulation)** allows the Arduino to simulate analog output by rapidly switching the digital pin on/off.
- By varying the duty cycle of each PWM pin, we can control the brightness of red, green, and blue LEDs.
- Mixing different brightness levels of RGB produces a wide range of colors (e.g., red + green = yellow).

### Use Cases:

- Mood lighting
- Color mixing experiments
- Visual indicators and displays

---